

## Lab2: Superposition theorem

### A. Objective

The objective of this experiment aims to analyze electric circuit using Superposition theorem. At the end of this experiment, the student will be able to construct and know how to analyze electric circuit.

### B. Instruments and Materials


- Adjustable DC power supply (1)
- Breadboard (1)
- DMM (Digital Multimeter) (1)
- $\frac{1}{2}$  watt resistors (1)

### C. Theory

• **Superposition:** According to this theorem, if there are two or more sources of EMFs acting simultaneously in a linear bilateral network, the current flowing through any section is the algebraic sum of all the currents that should flow in that section if each source of emf were considered separately and all other sources are replaced, for the time being, by their internal resistances.


### D. Circuit testing

- a. Nodal and loop analysis

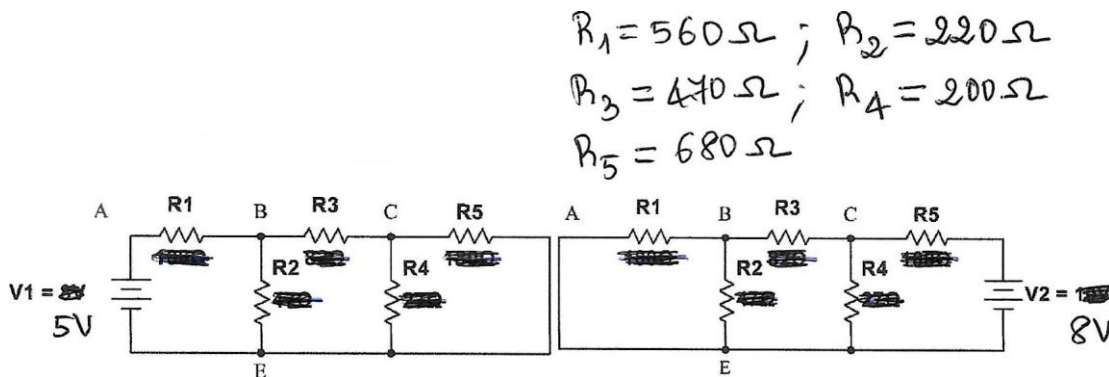

### E. Nodal and Loop Analysis

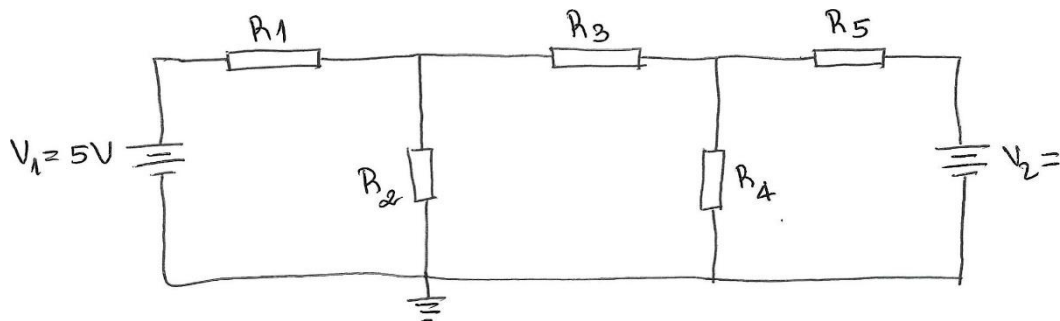1. Connect the circuit in Fig 1 with the given values;
2. Turn on the DC power supply and use DMM to measure the applied voltage (V1) 11V and (V2) 9V note the voltmeter readings;
3. Turn off the power supply and connect the circuit in Fig 1 with the DC power supply;



4. Turn on the power supply and measure the voltage on a node by using DMM. Record the results in Table 1;
5. Measure the value of current by using the ammeter. Note the readings of Ammeters and record the results in Table 1;

**Table1:**

Voltage(V)	V1 alone Present(Fig.1)			Voltage(V)	V2 alone Present(Fig.2)		
	Theoretical	Multisim	Experiment		Theoretical	Multisim	Experiment
$v_{R_1}$	3.586V		3.87V	$v_{R_1}$	0.447		0.87V
$v_{R_2}$	1.414V		1.13V	$v_{R_2}$	0.447		0.37V
$v_{R_3}$	1.064V		0.85V	$v_{R_3}$	1.323		0.73V
$v_{R_4}$	0.35V		0.28V	$v_{R_4}$	1.77		1.47V
$v_{R_5}$	0.35V		0.3V	$v_{R_5}$	6.23		6.46V
$I_{R1}$	0.88 mA		0.0069A	$I_{R1}$	8.9 mA		0.0015A
$I_{R2}$	2.03 mA		0.0051A	$I_{R2}$	6.42 mA		0.0016A
$I_{R3}$	2.91 mA		0.0018A	$I_{R3}$	2.48 mA		0.0015A
$I_{R4}$	8.85 mA		0.0013A	$I_{R4}$	1.75 mA		0.0072A
$I_{R5}$	11.76 mA		0.00044A	$I_{R5}$	1.75 mA		0.0096A

Voltage(V)	V3 alone Present(Fig.3)		
	Theoretical	Multisim	Experiment
$v_{R_1}$	2.93		5.83V
$v_{R_2}$	2.07		2.03V
$v_{R_3}$	0.19		0.74V
$v_{R_4}$	2.26		1.38V
$v_{R_5}$	5.74		3.55V
$I_{R1}$	5.2 mA		0.01051A
$I_{R2}$	9.4 mA		0.00922A
$I_{R3}$	0.4 mA		0.0016A
$I_{R4}$	11.3 mA		0.00684A
$I_{R5}$	8.44 mA		0.00531A

6. Verify the principle of superposition with the measured current. Will the principle of superposition apply to currents through each of the resistors?
7. Make the report using (Theoretical Vs Multisim Vs Experiment) results. Discuss the results of nodal and loop analysis with superposition.

**Discuss the result:** The experiment aimed to validate circuit analysis techniques, specifically nodal and loop analysis with the principle of superposition. While the tables present data for different voltage source configurations (V1, V2, and V3 alone, and presumably the combined case), a comprehensive conclusion requires comparing these individual contributions to the results when all sources are active.

