

## Lab1: Voltage and Current Sources

### A. Objective

The objective of this experiment is to achieve a stiff voltage source and a current source, which will be investigated.

### B. Instruments and Materials

1 Power supply: adjustable to 10V, 6  $\frac{1}{2}$ W resistors: 56 $\Omega$ , 200 $\Omega$ , 470 $\Omega$ , 2.2k $\Omega$ , and DMM (digital multimeter).

### C. Circuit testing

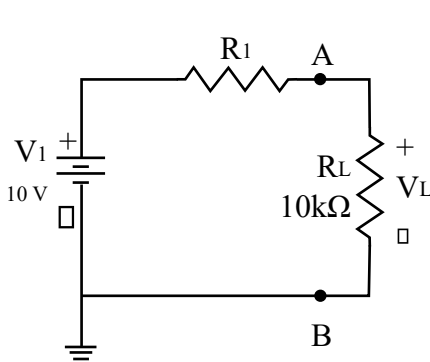


Figure 1

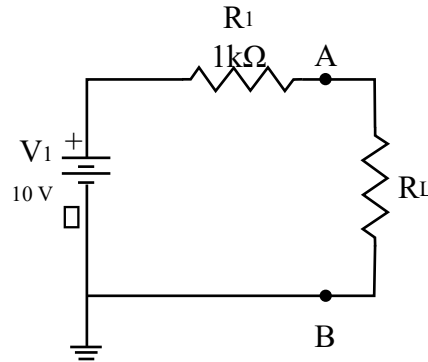


Figure 2

### D. Experimental Procedure

#### Voltage source

- The circuit left of AB terminals in Figure 1 represents a voltage source and its internal resistance  $R_1$ . Before measuring any voltage or current, the approximate value should be known so that the test equipment can be set to the proper range. Examine Figure 1 and estimate and record the load voltage for each value of  $R_1$  listed in Table 1. It is important to be able to estimate these rough values and to be able to calculate exact values.
- Sketch the circuit in Figure 1. Measure and record the value of each of the resistors used in this experiment. Build the circuit in Figure 1 using the values of  $R_1$  given in Table 1. Measure and adjust the source voltage to 10 V. For each  $R_1$  value, measure and record  $V_L$  in Table 1.

#### Current source

- The circuit left of the AB terminals in Figure 2 acts like a current source under certain conditions. Estimate and record the load current for each value of load resistance shown in Table 2.
- Sketch the circuit in Figure 2. Build the circuit of Figure 2 using the  $R_L$  values given in Table 2. Measure and adjust the source voltage to 10 V. For each  $R_L$  value, measure and record  $I_L$  in Table 2.

## Experiment 01

Resistor ( $\Omega$ )	Measured Value
56	56.1
200	198.1
470	460.2
10k	9.49k
2.2k	2.1k

Table 1: VOLTAGE SOURCE

$R_1$ ( $\Omega$ )	Estimate $V_L(V)$	Measured $V_L(V)$	
		Multisim	Actual
56	9.94		9.94
200	9.8		9.8
470	9.55		9.55
2.2k	8.19		8.17

Table 2: CURRENT SOURCE

$R_L$ ( $\Omega$ )	Estimate $I_L(A)$	Measured $I_L(A)$	
		Multisim	Actual
56	0.0046		4.4
200	0.00414		4.10
470	0.00379		3.73

. Formula for calculate:  $V_L = \frac{R_L}{R_1 + R_L} \times V$

. Formular for calculate:  $I_L = \frac{V}{R_1 + R_2}$

### **Questions**

1. The data of Table 1 prove that load voltage is:  
☐ Perfectly constant; ☐ small; ☐ heavily dependent on load resistance; ☐ approximately constant  
➤ **Answer:** Heavily dependent on load resistance.
2. When internal resistance  $R_1$  increases in Figure 1, load voltage:  
☐ increases slightly; ☐ decreases slightly; ☐ stays the same.  
➤ **Answer:** decreases slightly.
3. The circuit left of the AB terminals in Figure 2 acts approximately like a current source because the current values in Table 2:  
☐ increase slightly; ☐ are almost constant; ☐ decrease a great deal; ☐ depend heavily on  $R_L$   
➤ **Answer:** increase slightly.